

Power Electronics

Boost Converter

Taegeon Han & Jaehee Kim, Steel Hard
05/07/23

Question 1. From the PSIM Circuit of the Boost converter shown in Fig. 2, the inductor current has $\Delta i_L = 2A$. It is operating in dc steady state under the following conditions: $V_{in} = 5V$, $V_{out} = 12V$, $P_{out} = 11W$, and $f_s = 200kHz$.

(a) Assuming ideal components, calculate L and draw the waveforms of duty, MOSFET voltage, inductor current, diode current and capacitor current.

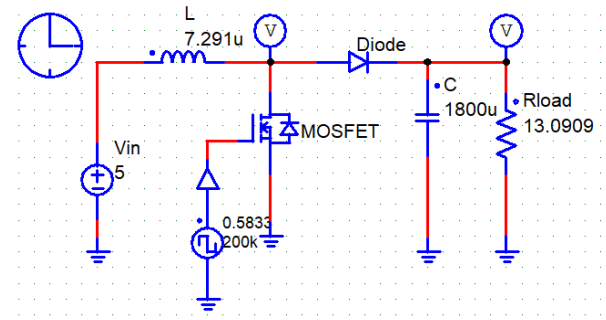


Figure 1. Circuit of Boost Converter

$$D = 1 - \frac{V_{in}}{V_{out}} = \frac{7}{12} \approx 0.5833$$

$$L = \frac{V_{in} \cdot D}{\Delta i_L \cdot f_s} = 7.291[\mu H]$$

$$R_{Load} = \frac{V_{out}^2}{P_{out}} = 13.0909[\Omega]$$

$$I_L = I_{in} = \frac{P_{in}}{V_{in}} = \frac{P_{out}}{V_{in}} = \frac{1}{V_{in}} \cdot \frac{V_{out}^2}{R_{Load}} = \frac{1}{V_{in}} \cdot \left(\frac{V_{in}}{1-D} \right)^2$$

$$= \frac{V_{in}}{(1-D)^2 \cdot R_{Load}} = 2.2[A]$$

$$I_{L(max)} = I_L + \frac{\Delta i_L}{2} = 3.2[A]$$

$$I_{L(min)} = I_L - \frac{\Delta i_L}{2} = 1.2[A]$$

$$I_{out} = \frac{V_{out}}{R_{Load}} = 0.9167[A]$$

$$T_{on} = D \cdot T_s = D \cdot \frac{1}{f_s} = 2.915[\mu s]$$

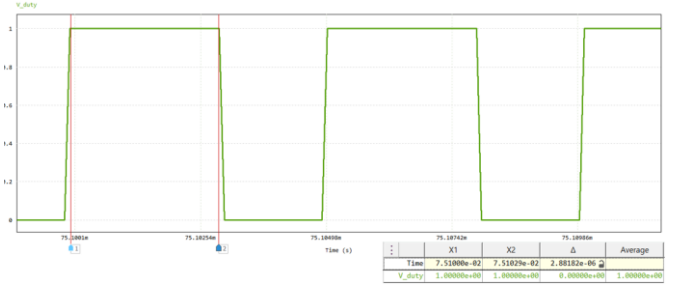


Figure 2. waveforms of duty

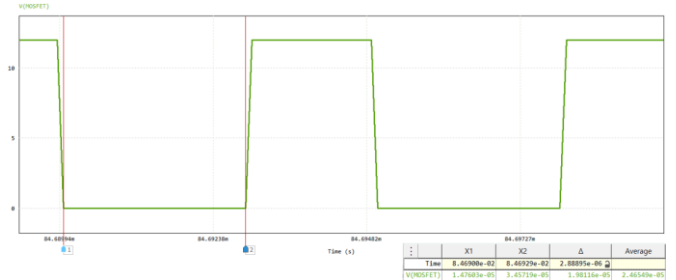


Figure 3. waveforms of MOSFET Voltage

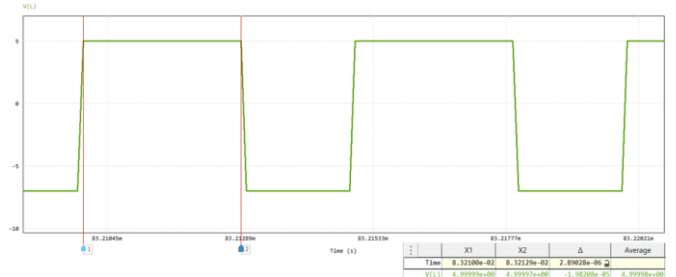


Figure 4. waveforms of Inductor Voltage

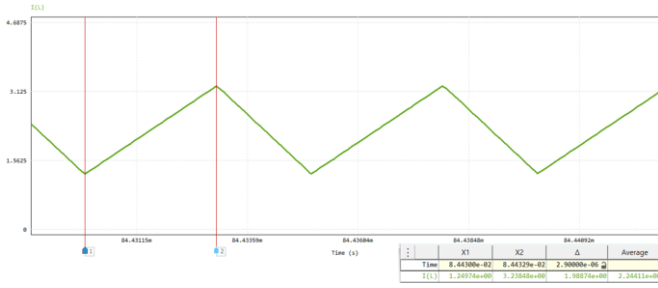


Figure 5. waveforms of Inductor Current

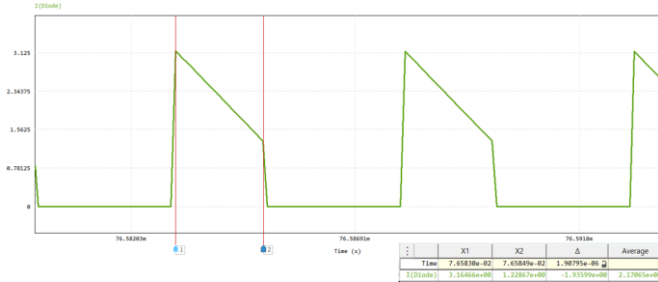


Figure 6. waveforms of Inductor Current

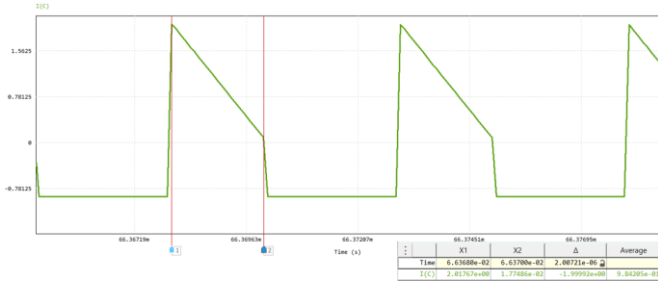


Figure 7. waveforms of MOSFET Current

Question 2. In a Boost converter, $L = 25 \mu\text{H}$. It is operating in dc steady state under the following conditions: $V_{in} = 12 \text{ V}$, $D = 0.4$, $P_{out} = 25 \text{ W}$, and $f_s = 400 \text{ kHz}$. Assume ideal components. Calculate the critical value of the output load R_{Load} and P_{out} below which the converter will enter the discontinuous conduction mode of operation.

$$V_{out} = \frac{1}{1-D} \times V_{in} = \frac{1}{1-0.4} \times 12 = 20[\text{V}]$$

To enter DCM of operation,

$$I_{L(crit)} = \Delta i_L = \frac{V_{in}}{2L} DT_s = 0.24[\text{A}]$$

$$P_{out(crit)} = P_{in} = V_{in} I_{in} = V_{in} I_{L(crit)} = 2.88[\text{W}]$$

$$R_{load} = \frac{P_{out(crit)}}{I_{L(crit)}^2} = 50[\Omega]$$

The equations and graphs above indicate that the theoretical values of voltage and current for the devices in the boost converter circuit are consistent with the simulation values.

Question 3. In the Boost converter from problem 2, the input voltage is varying in a range from 9V to 15 V. For each input value, the duty-ratio is controlled to keep the output voltage constant at its nominal value (with $V_{in} = 12$ V and $D = 0.4$). Calculate the critical value of the inductance L such that this Boost converter remains in the continuous conduction mode at and above $P_{out} = 5$ W under all values of the input voltage V_{in} . (Check Appendix)

```
명령 창
Result =
'Critical Value of Inductance is 14.81[uH] and it is when input voltage is 13.33[V]'
fx >>
```

Figure 9. MATLAB Results about Question 3

To remain CCM of operation,

$$I_L \geq I_{L(crit)} = \Delta i_L = \frac{V_{in}}{2L} DT_s$$

$$P_{in} = V_{in} I_{in} = V_{in} I_L = P_{out}$$

$$L \geq \frac{V_{in}^2}{2P_{out}} DT_s = \frac{V_{in}^2}{2P_{out}} \cdot \frac{1}{f_s} \left(1 - \frac{V_{in}}{V_{out}}\right)$$

$$V_{out} = \left(\frac{1}{1-D}\right) V_{in} = 20[V]$$

$$L_{crit} = \frac{V_{in}^2}{2 \cdot 5[W] \cdot 400[kHz]} \left(1 - \frac{V_{in}}{20[V]}\right)$$

The value we want to find is the value of L that operates as a CCM in all intervals of $9[V] \leq V_{in} \leq 15[V]$ when $P_{out}=5[W]$, so finding the maximum value of L will satisfy the conditions in all intervals.

The maximum value is the point where the gradient of the derivative becomes zero,

$$\frac{dL_{crit}}{dV_{in}} = \frac{V_{in}}{5[W] \cdot 400[kHz]} - \frac{3V_{in}^2}{2 \cdot 5[W] \cdot 400[kHz] \cdot 20[V]} = 0$$

$$V_{in} = 13.333[V]$$

$$\therefore L_{crit}(13.333) = 14.8148[\mu H]$$

Using MATLAB, we can also find the solution.

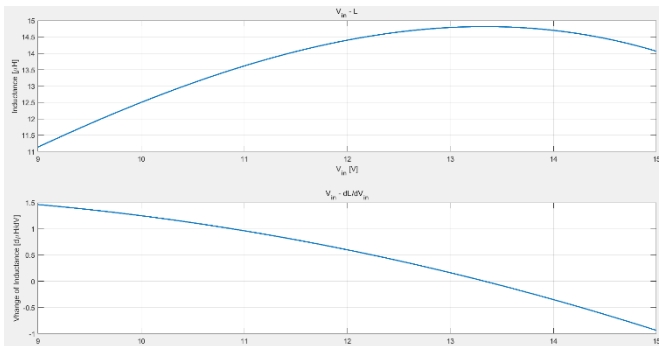


Figure 8. MATLAB Results about L_{crit} , dL_{crit}/dV_{in}

Question 4. A Boost converter is to be designed with the following values: $V_{in} = 5$ V, $V_{out} = 12$ V, and the maximum output power $P_{out} = 40$ W. The switching frequency is selected to be $f_s = 400$ kHz. Assume ideal components. Estimate the value of L if the converter is to remain in CCM at one-third the maximum output power.

$$V_{out} = \frac{1}{1-D} V_{in}, \quad D = \frac{7}{12} \approx 0.583$$

$$P_{out} = P_{in} = \frac{40}{3} [\text{W}]$$

To remain CCM of operation,

$$L \geq \frac{DD'^2}{2} RT_s$$

$$I_L = \frac{P_{out}}{V_{out}} = \frac{\frac{40}{3}}{12} = 1.11 [\text{A}]$$

$$R = \frac{V}{I_L} = \frac{12}{1.11} = 10.81 [\Omega]$$

$$\begin{aligned} \therefore L_{crit} &= \frac{DD'^2}{2f_s} R = \frac{0.583 \times (1 - 0.583)^2}{2 \times 400k} \times 10.81 \\ &= 1.37 [\mu\text{H}] \end{aligned}$$